

# Serial Arithmetic Processor

Deyvi Andrade- Aviles

*Department of Electrical and Computer Engineering, University of Massachusetts Lowell*  
Submitted: 22 December 2023

## **Abstract**

Serial arithmetic processors are a type of processor that performs operations on data one bit at a time, rather than processing multiple bits simultaneously like parallel processors. In this particular project, the design that is being constructed has specifications that would allow the user to perform a set of operations on a 4-bit operation code — OpCode. The design consists of three main modules; a data path, state generator, and a control circuit. These three modules will work in conjunction to output a 4-bit result.

## 1 State Transition Table

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Ut purus elit, vestibulum ut, placerat ac, adipiscing vitae, felis. Curabitur dictum gravida mauris. Nam arcu libero, nonummy eget, consectetur id, vulputate a, magna. Donec vehicula augue eu neque. Pellentesque habitant morbi tristique senectus et netus et malesuada fames ac turpis egestas. Mauris ut leo. Cras viverra metus rhoncus sem. Nulla et lectus vestibulum urna fringilla ultrices. Phasellus eu tellus sit amet tortor gravida placerat. Integer sapien est, iaculis in, pretium quis, viverra ac, nunc. Praesent eget sem vel leo ultrices bibendum. Aenean faucibus. Morbi dolor nulla, malesuada eu, pulvinar at, mollis ac, nulla. Curabitur auctor semper nulla. Donec varius orci eget risus. Duis nibh mi, congue eu, accumsan eleifend, sagittis quis, diam. Duis eget orci sit amet orci dignissim rutrum.

Table 1: Truth table with inputs  $Q_3, Q_2, Q_1, Q_0$ , and outputs  $Q_3^+ Q_2^+ Q_1^+ Q_0^+$  representing the "next states" of the 4-digit inputs. Note that the PS stands for "Present States".

$OpCode[3:0]$	$MUX_{OUT}$	$x_i$	$y_i$	$c_0$	<i>Instruction</i>
0 0 0 0	$c_0$	$A_i$	0	1	dec: $A - 1 \rightarrow A$
0 0 0 1	$c_0$	$A_i$	1	0	inc: $A + 1 \rightarrow A$
0 0 1 0	$c_0$	$A_i$	$B_i$	0	add: $A + B \rightarrow A$
0 0 1 1	$c_0$	$A_i$	$\overline{B_i}$	1	sub: $A - B \rightarrow A$
0 1 0 1	$c_1$	$A_i$	1	0	and: $A \& B \rightarrow A$
1 0 1 0	$c_2$	$A_i$	$B_i$	0	comp: $\overline{A} \rightarrow A$
1 1 1 1	$c_3$	$A_i$	$\overline{B_i}$	1	or: $A \mid B \rightarrow A$

## Stage Generator

Table 2: Truth table with inputs  $Q_3, Q_2, Q_1, Q_0$ , and outputs  $Q_3^+ Q_2^+ Q_1^+ Q_0^+$  representing the "next states" of the 4-digit inputs. Note that the PS stands for "Present States".

$PS$	$START$	s1rA s0rA	s1rB s0rB	$CSEL$	$CE$
$T_0$	0	0 0	0 0	$d$	0
$T_0$	1	1 1	$d d$	$d$	$d$
$T_1$	$d$	0 0	1 1	1	1
$T_2$	$d$	0 1	0 1	0	1
$T_3$	$d$	0 1	0 1	0	1
$T_4$	$d$	0 1	0 1	0	1
$T_5$	1	0 0	0 0	$d$	0
$T_5$	0	0 1	0 1	0	1