

# Serial Arithmetic Processor

Deyvi Andrade- Aviles

*Department of Electrical and Computer Engineering, University of Massachusetts Lowell*  
Submitted: 22 December 2023

## **Abstract**

Serial arithmetic processors are a type of processor that performs operations on data one bit at a time, rather than processing multiple bits simultaneously like parallel processors. In this particular project, the design that is being constructed has specifications that would allow the user to perform a set of operations on a 4-bit operation code — OpCode. The design consists of three main modules; a data path, state generator, and a control circuit. These three modules will work in conjunction to output a 4-bit result.

## 1 Design

### DATAPATH Module

**ALU Function Set** This particular module specifications include two registers that corresponds to one 4-digit bit. These registers have control inputs **s1rA** and **s0rA** for register A, and **s1rB** **s0rB** for register B. These registers sport a 74194 chip that are used as shift/parallel load registers. Towards the center of the diagram is where the single 2:1 input processor multiplexer is located. The bottom right portion of the diagram features the carry portion of the full adder (which is located towards the left of item labeled **CARRY MUX**).

In addition to the hardware, the module also includes inputs which are employed in hopes of inputting the proper configuration for the machine once it is “powered on”. Note that the machine is also configured with asynchronous active-low reset (**rst** as seen in the diagram) CLK is simply the clock input meant to keep track of the different stages the machine may be in during its operation. **CS** and **CSEL** represent the carry MUX selector bits and the carry enable respectively.

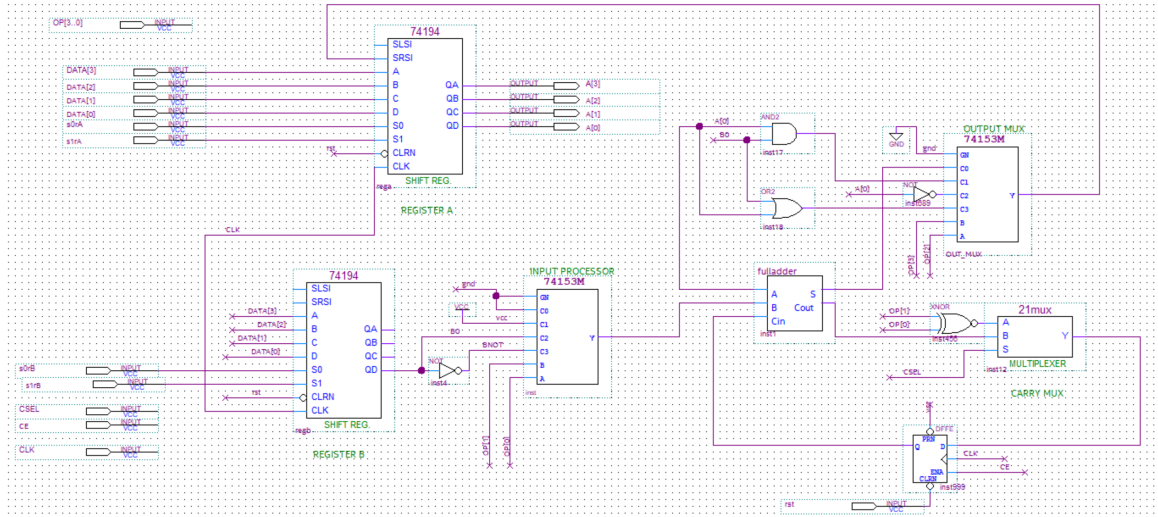


Figure 1: Block diagram schematic of the DATAPATH module in Quartus Prime. The design includes inputs that are fed into registers, muxes, input processors, etc.

**DATAPATH Table** The following table was derived from the DATAPATH module.

Table 1: Truth table that was derived from the DATAPATH module. The inputs are the 4-bit OpCodes that each represent a unique operation. This operation corresponds to a certain instruction which is listed on the far right column of the table. Note that the outputs for  $x_i$  and  $y_i$  each represent the 4-bit value for A and B; which make up the two integers whom of which are being operated on.

$OpCode[3:0]$	$MUX_{OUT}$	$x_i$	$y_i$	$c_0$	Instruction
0 0 0 0	$c_0$	$A_i$	0	1	dec: $A - 1 \rightarrow A$
0 0 0 1	$c_0$	$A_i$	1	0	inc: $A + 1 \rightarrow A$
0 0 1 0	$c_0$	$A_i$	$B_i$	0	add: $A + B \rightarrow A$
0 0 1 1	$c_0$	$A_i$	$\overline{B_i}$	1	sub: $A - B \rightarrow A$
0 1 0 1	$c_1$	$A_i$	1	0	and: $A \& B \rightarrow A$
1 0 1 0	$c_2$	$A_i$	$B_i$	0	comp: $\overline{A} \rightarrow A$
1 1 1 1	$c_3$	$A_i$	$\overline{B_i}$	1	or: $A - B \rightarrow A$

## Stage Generator

**State Diagram** As stated prior, this machine is configured to have an asynchronous reset; in doing so, the machine needs to be able to decide what operations it must be accomplishing. Figure 2 depicts an interpretation of the ASM chart of the serial arithmetic processor. The diagram depicts the different states that the machine may undergo during its operation. Note the implicit timing information that is denoted by box which indicates exactly what operation the machine is undergoing during said state (denoted by  $T_i$  where  $i$  represents a state from 1-5).

 


Figure 2: State diagram for the serial arithmetic processor. The ASM for this machine can be summed up in the following sentences: Hold in the initial state ( $T_0$ ) until **START** is set to 1. Move through the remaining 5 states and return to  $T_0$  when completed. The value of **START** does not matter while in states 1-4. The system will pause in  $T_5$  if **START** is left at 1, and will only return to  $T_0$  if **START** = 0. Asynchronously return to the initial state ( $T_0$ ) when the system **RESET** is '0'

**State Table & Formulas** The following is the state table and the formulas derived from the State table. Note that the inputs for the table are  $PS$  and  $START$

Table 2: State Table

$PS$	$START$	$NS$
$T_0$	0	$T_0$
$T_0$	1	$T_1$
$T_1$	$x$	$T_2$
$T_2$	$x$	$T_3$
$T_3$	$x$	$T_4$
$T_4$	$x$	$T_5$
$T_5$	1	$T_5$
$T_5$	0	$T_0$

$$\begin{aligned}
 DFF &\rightarrow D_0 = T_0^+ \\
 D_1 &= T_0 \cdot START \\
 D_2 &= T_1 \\
 D_3 &= T_2 \\
 D_4 &= T_3 \\
 D_5 &= T_4 + (T_5 \cdot START)
 \end{aligned}$$

**State Generator Block Diagram Schematic** The first diagram shown in this project is of the state generator. The main function behind this module is to generate the state in which the machine is operating in. Note that the clock is wired asynchronously.

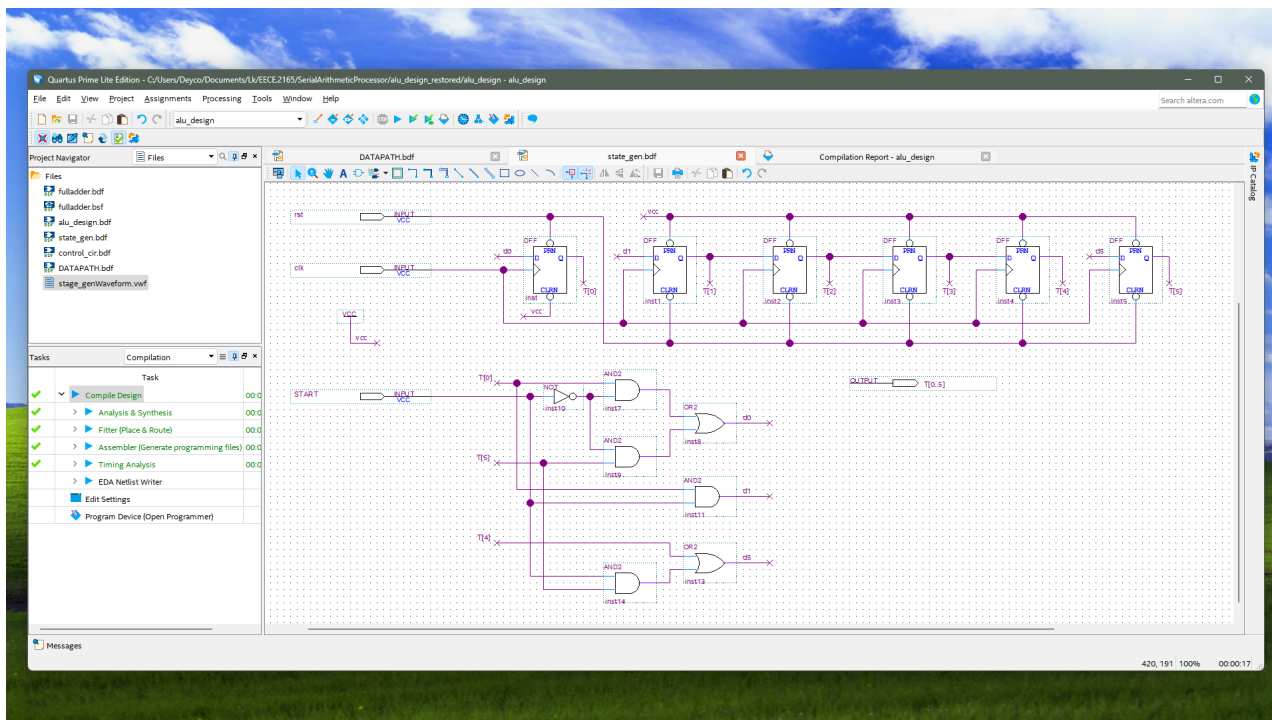


Figure 3: Block diagram figure of the state generator module used in the serial arithmetic processor in Quartus Prime.

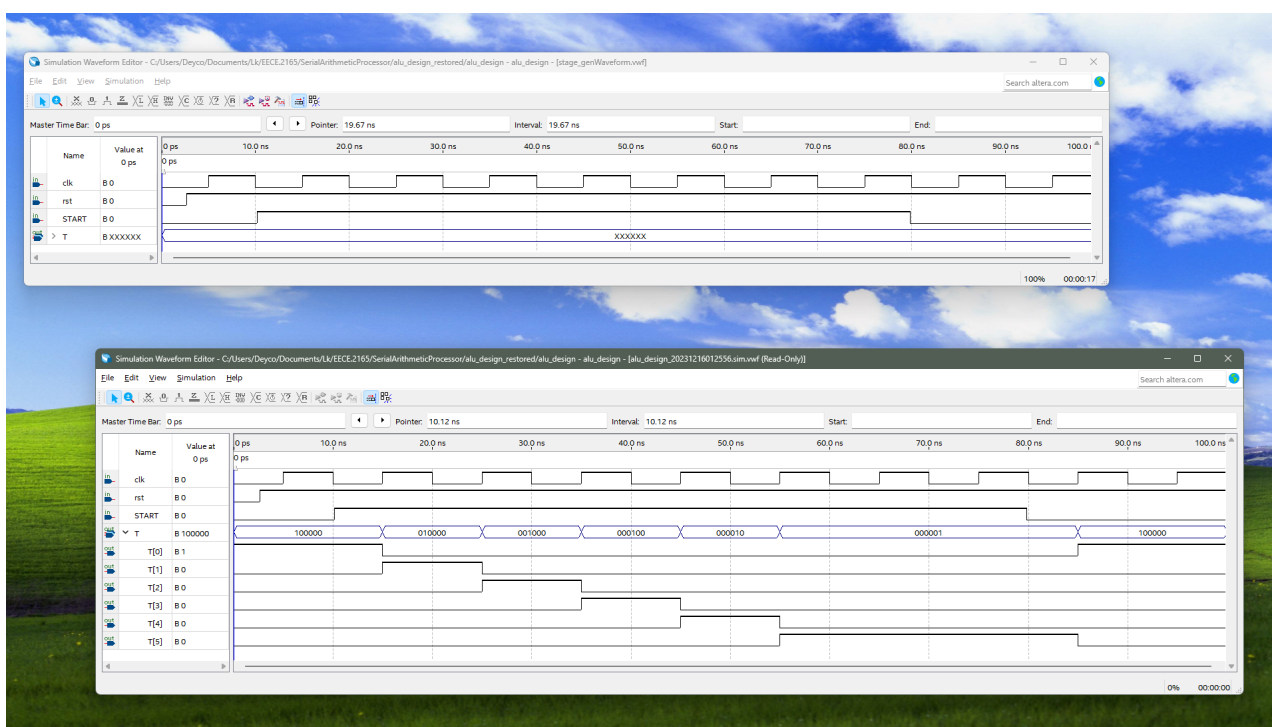


Figure 4: Waveform diagram of the state generator module indicating that the module is functioning as intended.

Table 3: filler

$PS$	$START$	s1rA s0rA	s1rB s0rB	$CSEL$	$CE$
$T_0$	0	0 0	0 0	$d$	0
$T_0$	1	1 1	$d d$	$d$	$d$
$T_1$	$d$	0 0	1 1	1	1
$T_2$	$d$	0 1	0 1	0	1
$T_3$	$d$	0 1	0 1	0	1
$T_4$	$d$	0 1	0 1	0	1
$T_5$	1	0 0	0 0	$d$	0
$T_5$	0	0 1	0 1	0	1